


General Class Unit 5

Question Pool §5



Electrical Principles


3 Questions

© 2013–2019 By New England Amateur Radio, Inc.


New England Amateur Radio Inc.

Amateur Radio General License Course

2



Impedance



Impedance is a measure of *the opposition to the flow of current in an AC circuit.*

Impedance is measured in Ohms (Ω) and represented by the letter *Z*.

Impedance matching of a power source to an electrical load is important because then *the source can deliver maximum power to the load.*

Impedance is the sum of resistance and reactance.


© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.


Amateur Radio General License Course

3

G5A01 G5A07



Reactance



Reactance is the opposition to the flow of alternating current caused by capacitance or inductance.



Reactance is measured in *Ohms* (Ω).

In an inductor as *the frequency of the applied AC increases, the reactance increases.*

Inductors block AC and pass DC.

In a capacitor as *the frequency of the applied AC increases, the reactance decreases.*

Capacitors block DC and pass AC.


© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.


Amateur Radio General License Course

4


G5A03/G5A04 G5A02 G5A09
G5A05 G5A06



Impedance Matching



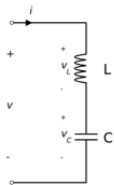A method of matching impedance is to *insert an LC network between the two circuits.*




© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.


Amateur Radio General License Course

5

G5A11



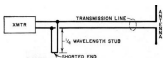
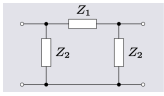

Impedance Matching



When needing to match impedances, one can use:

- A length of transmission line.*
- A Pi-network or π -network.*
- A transformer.*


One reason to use an impedance matching transformer *to maximize the transfer of power.*


© 2013–2019 By New England Amateur Radio, Inc.
New England Amateur Radio Inc.
Amateur Radio General License Course


6

G5A10 G5A08
Z1 is usually an inductor. Z2 is usually a capacitor.



Ohm's and Watt's Laws



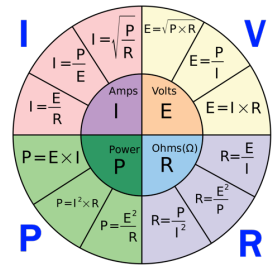


Power, Voltage, Current & Resistance Calculator


© 2013–2019 By New England Amateur Radio, Inc.
New England Amateur Radio Inc.
Amateur Radio General License Course

22

(G5B04)



Ohm's and Watt's Laws



Ohm's Law

$$E = IR$$

$$I = \frac{E}{R}$$

$$R = \frac{E}{I}$$

Watt's Law

$$P = IE$$


$$P = I^2 R$$

$$E = \sqrt{PR}$$


© 2013–2019 By New England Amateur Radio, Inc.
New England Amateur Radio Inc.
Amateur Radio General License Course

23

(G5B04)



Power Example



$$P = \frac{E^2}{R}$$

How many watts of electrical power are used if 400 VDC is supplied to an 800-ohm load?

$$P = \frac{(400V)(400V)}{800\Omega}$$

© 2013–2019 By New England Amateur Radio, Inc.
New England Amateur Radio Inc.
Amateur Radio General License Course

27



Power Example



28

$$P = \frac{E^2}{R}$$

How many watts of electrical power are used if 400 VDC is supplied to an 800-ohm load?

$$P = \frac{160000V^2}{800\Omega}$$

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course



Power Example



29

G5B03 (G5B012)

$$P = \frac{E^2}{R}$$

How many watts of electrical power are used if 400 VDC is supplied to an 800-ohm load?

$$P = 200W$$

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course



Power Example



34

$$P = I^2 R$$

How many watts are dissipated when a current of 7.0 milliamperes flows through 1,250 ohms?

$$P = (0.007A)^2 \times 1250\Omega$$

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course



Power Example



35

$$P = I^2 R$$

How many watts are dissipated when a current of 7.0 milliamperes flows through 1,250 ohms?

$$P = 0.000049A^2 \times 1250\Omega$$

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course



Power Example

$$P = I^2 R$$

How many watts are dissipated when a current of 7.0 milliamperes flows through 1,250 ohms?

$$P = 0.06125W$$



36



Power Example

$$P = I^2 R$$

How many watts are dissipated when a current of 7.0 milliamperes flows through 1,250 ohms?

$$P = 61.25mW$$




37

G5B05



Measuring AC Voltages

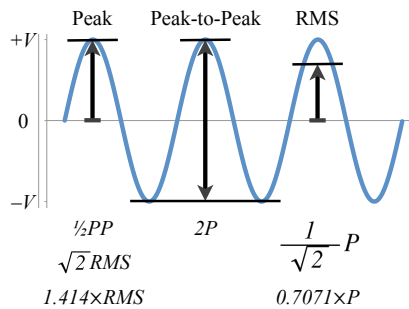

39

(G5B07 G5B08 G5B09)




PEP & PP

Peak envelope power (PEP) is calculated using the RMS voltage in Watt's Law.

The ratio of peak envelope power to average power is 1.00 for an unmodulated carrier.

An unmodulated carrier gives a straight RF carrier wave, so the average and peak envelope voltages are the same, so the ratio is 1:1 or 1.00.

$$PEP = \frac{(V_{RMS})^2}{R}$$

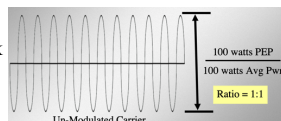

41

G5B11



PEP & PP



42

G5B06 (G5B13 G5B14)

What is the output PEP from a transmitter if an oscilloscope measures 200 volts peak-to-peak across a 50-ohm dummy load connected to the transmitter output?

So we know $E_{PP} = 200V$ and $R = 50\Omega$, but we need E_{RMS} .

$$E_p = \frac{1}{2} E_{PP} = \frac{1}{2} 200V = 100V$$

$$E_{RMS} = \frac{1}{\sqrt{2}} E_p = 0.7071 E_p = 0.7071 \times 100V = 70.71V$$

$$P = \frac{E_{RMS}^2}{R} = \frac{(70.71V)^2}{50\Omega} = \frac{5000V^2}{50\Omega} = 100W$$

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course



Decibels



44

G5B01 G5B10

Decibels measure the ratio of change between two values.

They are used to talk about a large range of values.

$$dB = 10 \log \left(\frac{P_1}{P_2} \right) \quad P_1 = 10^{\frac{dB}{10}} P_2$$

A factor of two increase or decrease in power results in *approximately 3 dB* change.

A 1 dB line loss would result in a *20.6 percent* power loss.

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course



Parallel and Series Circuits




62


G5B02

A parallel circuit allows each component to have the same voltage potential across each component.

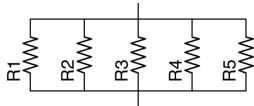The total current through a parallel circuit is *the sum of the currents through each branch*.



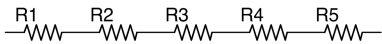A series circuit has each component connected along a single path, so each component has the same current passing through it.



© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course



Parallel and Series Circuits



63

How do you calculate the total value of a circuit when you arrange a type of component together in a parallel or series circuit?

The total value of a set of components can be calculated using one of two equations:


$$N_{Total} = N_1 + N_2 + \dots + N_n$$

$$N_{Total} = \frac{1}{\frac{1}{N_1} + \frac{1}{N_2} + \dots + \frac{1}{N_n}}$$

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course




Parallel and Series Circuits



$$N_{Total} = N_1 + N_2 + \dots + N_n$$

Add the values of each component together.

Used for:

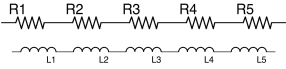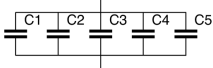- Resistors in series
- Inductors in series
- Capacitors in parallel




© 2013–2019 By New England Amateur Radio, Inc.
New England Amateur Radio Inc.
Amateur Radio General License Course

64

G5C03 G5C13 G5C14 (G5C05
G5C08 G5C11)




Parallel and Series Circuits

$$N_{Total} = \frac{I}{\frac{1}{N_1} + \frac{1}{N_2} + \dots + \frac{1}{N_n}}$$


When dealing with only two components this can be simplified to:

$$N_{Total} = \frac{N_1 N_2}{N_1 + N_2}$$



© 2013–2019 By New England Amateur Radio, Inc.
New England Amateur Radio Inc.
Amateur Radio General License Course

65




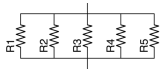
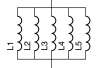
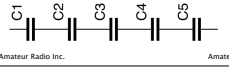
Parallel and Series Circuits

$$N_{Total} = \frac{I}{\frac{1}{N_1} + \frac{1}{N_2} + \dots + \frac{1}{N_n}} \quad N_{Total} = \frac{N_1 N_2}{N_1 + N_2}$$

Used for:


- Resistors in parallel
- Inductors in parallel
- Capacitors in series



© 2013–2019 By New England Amateur Radio, Inc.
New England Amateur Radio Inc.
Amateur Radio General License Course


66



Parallel Resistor Calculation

$$N_{Total} = \frac{I}{\frac{1}{N_1} + \frac{1}{N_2} + \dots + \frac{1}{N_n}}$$

What is the total resistance of a 10 ohm, 20 ohm, and 50 ohm resistor in parallel?



© 2013–2019 By New England Amateur Radio, Inc.
New England Amateur Radio Inc.
Amateur Radio General License Course

69

G5C15 (G5C04 G5C09 G5C10)



Series Capacitor Calculation



71

$$N_{Total} = \frac{N_1 N_2}{N_1 + N_2}$$

What is the capacitance of a 20 microfarad capacitor in series with a 50 microfarad capacitor?

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.


Amateur Radio General License Course



Transformers



82

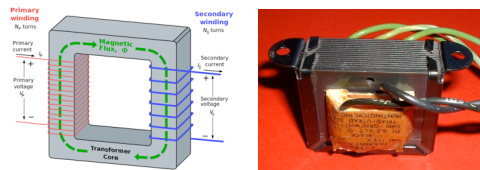

Transformers have a primary and a secondary winding.
The primary winding is connected to the incoming source of energy.

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course




Transformers



83

G5C01

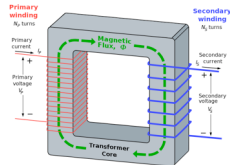

Transformers work by *mutual inductance* between the primary and secondary windings.

RMS voltage and current between the primary and secondary windings are related to the ratio of the number of windings.

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course




Transformers



85

G5C02

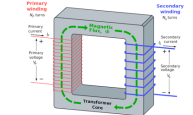


$$\frac{E_P}{E_S} = \frac{N_P}{N_S} = a$$

The ratio of the primary and secondary voltages are the same as the ratio of the number of windings of wire.

If $a > 1$, it is a step-down transformer;
if $a < 1$, it is a step-up transformer.

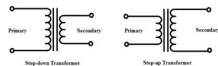If a signal is applied to the secondary winding of a 4:1 voltage step-down transformer instead of the primary winding, *the output voltage is multiplied by 4.*



© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course




Transformers



86

G5C16

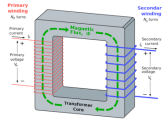

$$\frac{E_P}{E_S} = \frac{N_P}{N_S} = a$$

The conductor of the primary winding of many voltage step-up transformers is larger in diameter than the conductor of the secondary winding *to accommodate the higher current of the primary*.

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.


Amateur Radio General License Course



Transformers



88

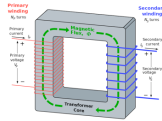

$$\frac{E_P}{E_S} = \frac{N_P}{N_S} = a$$

$$Z_P = a^2 Z_S \quad a = \sqrt{\frac{Z_P}{Z_S}}$$

A transformer can also be used for impedance matching.

Impedance matching through a transformer is related to the square of the ratio of the windings.

Transformers are often used to match audio (speaker) or RF (antenna) impedance between sources and loads.

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course



Transformers



90

G5C06

What is the RMS voltage across a 500-turn secondary winding in a transformer if the 2250-turn primary is connected to 120 VAC?

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course



Transformers



92

G5C07

What is the turns ratio of a transformer used to match an audio amplifier having a 600 ohm output impedance to a speaker having a 4 ohm impedance?

© 2013–2019 By New England Amateur Radio, Inc.

New England Amateur Radio Inc.

Amateur Radio General License Course